



Assignment 3: CS220

Sequence Detector and 3-bit Odd Parity Bit Generator Using FSM

Abhishek Pardhi, Aayush Kumar, Jahnavi Kairamkonda

200026, 200008, 200482

B.Tech students

apardhi20@iitk.ac.in, akgarg20@iitk.ac.in,
kjahnavi20@iitk.ac.in

INDIAN INSTITUTE OF TECHNOLOGY
KANPUR

DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING

February 17, 2022

Contents

1	Sequence Detector	1
1.1	Description	1
1.2	State Diagram	1
1.3	State Table	2
1.4	Excitation Table	2
1.5	K-map	2
1.6	Circuit Diagram	3
2	3-bit Odd Parity Bit Generator	4
2.1	Description	4
2.2	State Diagram	4
2.3	State Table	5
2.4	Excitation Table	5
2.5	K-map	5
2.6	Circuit Diagram	6

1 Sequence Detector

1.1 Description

The sequence detector is made using *Mealy FSM Machine*. Sequence to be detected is **1010**. We've used **four states** to build the state machine: **IDLE**(2'b00), **b**(2'b10), **c**(2'b01) and **d**(2'b11). To make the sequence detector *overlapping* we took care of the transitions involved in making the state diagram. For the circuit, we've used two D Flip-Flops **D_x** and **D_y** to store the current state **XY** ($X = D_x$ & $Y = D_y$).

1.2 State Diagram

 


Figure 1: State diagram of sequence detector

1.3 State Table

PS	NS, O/P	
	x_1	
	0	1
00	(00,0)	(10,0)
01	(00,0)	(11,0)
10	(01,0)	(10,0)
11	(01,1)	(10,0)

Table 1: State table

1.4 Excitation Table

P.S.	P.S.	I/P	N.S.	N.S.	FF's	FF's	O/P
X	Y		X'	Y'	D_x	D_Y	
0	0	0	0	0	0	0	0
0	0	1	1	0	1	0	0
0	1	0	0	0	0	0	0
0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	0
1	0	1	1	0	1	0	0
1	1	0	0	1	0	1	1
1	1	1	1	0	1	0	0

Table 2: Excitation table

1.5 K-map

I	XY	00	01	11	10
		0	0	0	0
0		0	0	0	0
1		1	1	1	1

(a) D_x

XY	00	01	11	10
I				
0	0	0	1	1
1	0	1	0	0

(b) D_y

		XY			
		00	01	11	10
I	0	0	0	1	0
	1	0	0	0	0

(c) Z

Figure 2: K -maps

$$\Rightarrow D_x = I$$

$$\Rightarrow D_y = I'XY' + IX'Y + I'XY = I'X + IX'Y$$

$$\Rightarrow Z = I'XY$$

1.6 Circuit Diagram

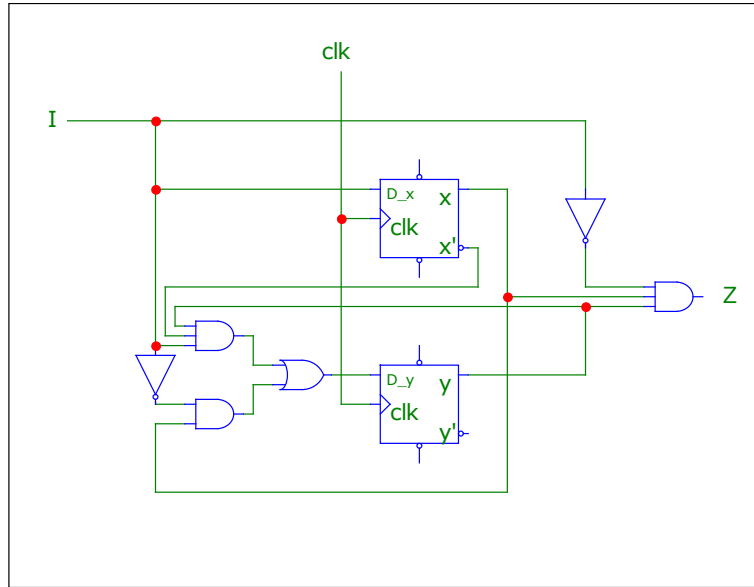


Figure 3: Circuit diagram of sequence detector

2 3-bit Odd Parity Bit Generator

2.1 Description

The odd parity bit generator was made using *Moore FSM Machine*. We've used **three states** to build the state machine: **IDLE(2'b00)**, **a(2'b01)** and **b(2'b10)**. For the circuit, we've used one D Flip-Flop D_x to store the current state X ($X = D_x$). The state machine starts at the state *IDLE* and then goes to the state *a* if input is 1 or goes to *b* if input is 0 else it stays in state *IDLE* if input is a white space. After going to state *a* or *b* the state machine stays at the same state if the input is 0 or goes to the other state(from *a* to *b* or vice versa) else goes to state *IDLE* if the input is a white space. Since this is a Moore machine, it will give an output of 1 when it is in state *b*(2'b10) otherwise will give 0 as output in other states.

2.2 State Diagram

 


Figure 4: State diagram of odd parity bit generator

2.3 State Table

PS	NS, O/P	
	x_1	
	0	1
0	(0,0)	(1,1)
1	(1,1)	(0,0)

Table 3: State table

2.4 Excitation Table

P.S.	I/P	N.S.	FF's	O/P
X		X'	D_x	(at P.S.)
0	0	0	0	0
0	1	1	1	0
0	0	0	0	0
0	1	1	1	0

Table 4: Excitation table

2.5 K-map

 


Figure 5: *K-maps*

$$\Rightarrow D_x = I'X + IX' = I \oplus X$$

$$\Rightarrow Z = X$$

2.6 Circuit Diagram

 


Figure 6: Circuit diagram of odd parity bit generator