



---

## Assignment 4: CS220

### *3-bit Gray code counter and 8-bit Adder/Subtractor Using FSM*

---

Abhishek Pardhi, Aayush Kumar, Jahnavi Kairamkonda

200026, 200008, 200482

B.Tech students

apardhi20@iitk.ac.in, akgarg20@iitk.ac.in,  
kjahnavi20@iitk.ac.in

INDIAN INSTITUTE OF TECHNOLOGY  
KANPUR

DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING

March 6, 2022

# Contents

<b>1</b>	<b>3-bit Gray code counter</b>	<b>1</b>
1.1	State Diagram . . . . .	1
1.2	State Assignment Table . . . . .	1
1.3	State Table . . . . .	2
1.4	Excitation Table . . . . .	2
1.5	K-map . . . . .	3
1.6	Circuit Diagram . . . . .	4
<b>2</b>	<b>8-bit Adder/Subtractor</b>	<b>5</b>
2.1	Description . . . . .	5
2.2	Circuit Diagram . . . . .	5

# 1 3-bit Gray code counter

## 1.1 State Diagram

 


Figure 1: State diagram of sequence detector

## 1.2 State Assignment Table

State Assignment	
S <sub>0</sub>	000
S <sub>1</sub>	001
S <sub>2</sub>	011
S <sub>3</sub>	010
S <sub>4</sub>	110
S <sub>5</sub>	111
S <sub>6</sub>	101
S <sub>7</sub>	100

Table 1: State Assignment table

### 1.3 State Table

PS	NS
000	001
001	011
011	010
010	110
110	111
111	101
101	100
100	000

Table 2: State table

### 1.4 Excitation Table

P.S.	P.S.	P.S.	N.S.	N.S.	N.S.	FF's	FF's	FF's	O/P
$X$	$Y$	$Z$	$X'$	$Y'$	$Z'$	$T_x$	$T_Y$	$T_Z$	
0	0	0	0	0	1	0	0	1	0
0	0	1	0	1	1	0	1	0	0
0	1	1	0	1	0	0	0	1	0
0	1	0	1	1	0	1	0	0	0
1	1	0	1	1	1	0	0	1	0
1	1	1	1	0	1	0	1	0	0
1	0	1	1	0	0	0	0	1	0
1	0	0	0	0	0	1	0	0	1

Table 3: Excitation table

## 1.5 K-map

Z \ XY	00	01	11	10
0	0	1	0	1
1	0	0	0	0

(a)  $T_x$

Z \ XY	00	01	11	10
0	0	0	0	0
1	1	0	1	0

(b)  $T_y$

Z \ XY	00	01	11	10
0	1	0	1	0
1	0	1	0	1

(c)  $T_z$

Z \ XY	00	01	11	10
0	0	0	0	1
1	0	0	0	0

(d)  $O$

Figure 2: *K-maps*

$$\Rightarrow T_x = \overline{Z}(X \oplus Y)$$

$$\Rightarrow T_y = Z(\overline{X} \oplus Y)$$

$$\Rightarrow T_z = \overline{Z} \oplus (X \oplus Y)$$

$$\Rightarrow O = XY\overline{Z} \cdot T_x \overline{T_y} \overline{T_z}$$

## 1.6 Circuit Diagram

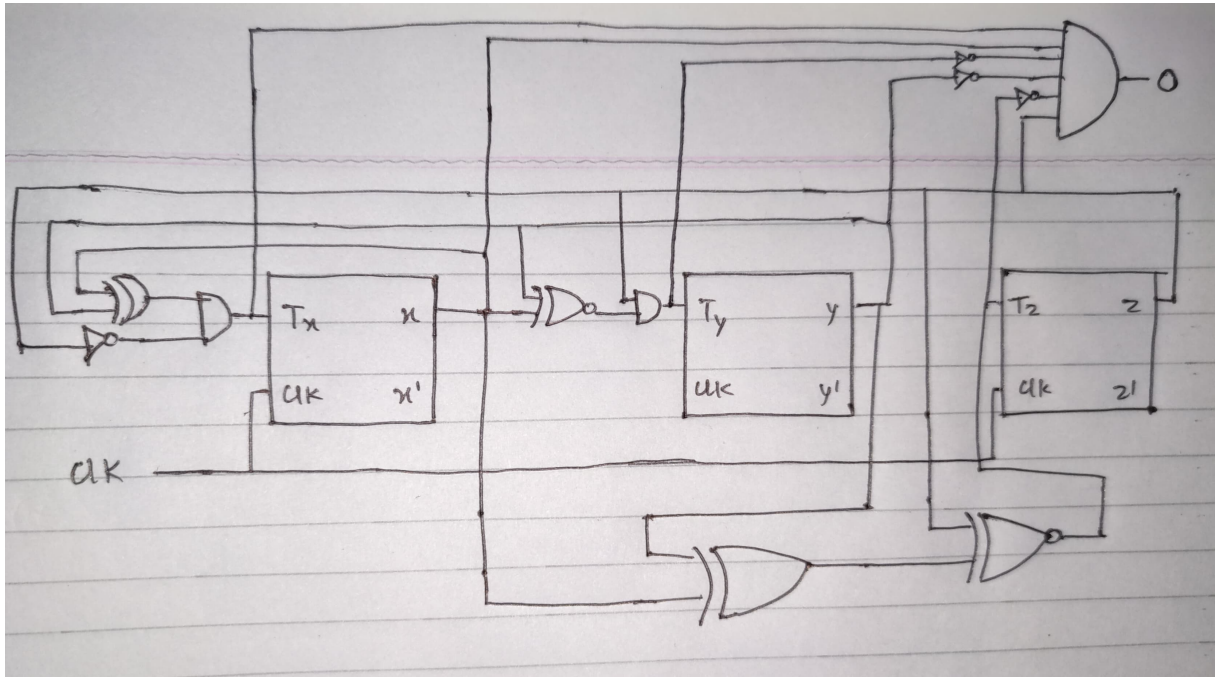


Figure 3: Circuit diagram of 3-bit Gray code counter

## 2 8-bit Adder/Subtractor

### 2.1 Description

The 8-bit adder/subtractor was made using eight 1-bit adder/subtractor. Each 1-bit adder/subtractor takes three 1-bit inputs **a**, **b**, **cin**, **opcode** and gives two 1-bit outputs sum and carry. We first made a full adder and then gave it **a** and  $\mathbf{b} \oplus \mathbf{opcode}$  as input. Here,  $\mathbf{b} \oplus \mathbf{opcode}$  gives us the 1's complement of **b** whenever **opcode** is 1'b1 (since XOR gate can invert or not invert a Boolean bit depending on input at other terminal). Also, we gave **opcode** as **cin** to the lower most significant bit's adder to convert the 1's complement of **b** to 2's complement of **b** (since 2's complement is obtained by flipping all bits of the binary number and adding 1).

The 8-bit adder/subtractor takes two 8-bit inputs **A** & **B** and one 1-bit input **opcode** and it gives one 8-bit output **Sum** if there's no overflow. The overflow is known from the value of  $\mathbf{cout}[7] \oplus \mathbf{cout}[6]$  (since overflow occurs whenever the carry out of last bit is not equal to carry out of second last bit).

### 2.2 Circuit Diagram

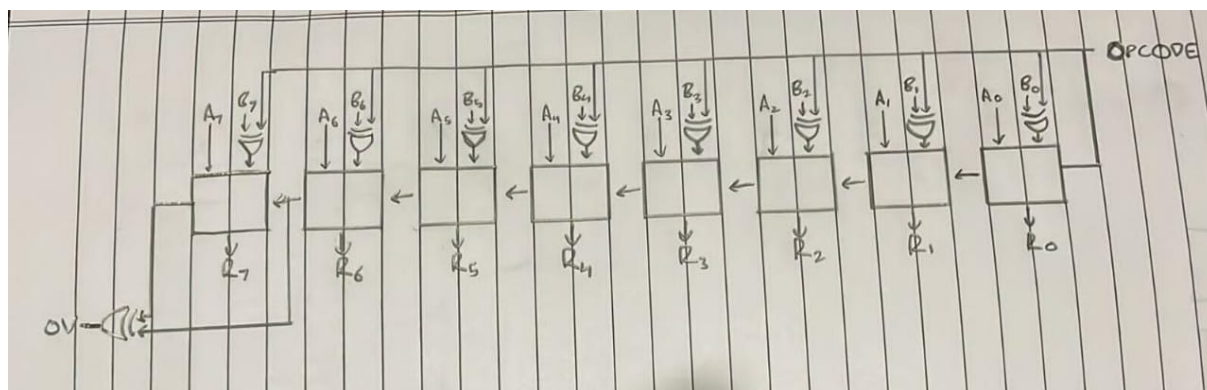


Figure 4: Circuit diagram of 8-bit Adder/Subtractor